

## Exercise 5: Logic Circuit Design

### SECTION A







1. Logic diagrams and truth tables are equally powerful in expressing the processing of gates and circuits. **(True/False)**
2. Boolean expressions are more powerful than logic diagrams in expressing the processing of gates and circuits. **(True/False)**
3. A NOT gate accepts two inputs.
4. The output value of an AND gate when both inputs are 1 is 1. **(True/False)**
5. The AND and OR gates produce opposite results for the same input **(True/False)**
6. The output value of an OR gate when both inputs are 1 is 1. **(True/False)**
7. The output of an OR gate when one input is 0 and one input is 1 is 0. **(True/False)**
8. The output value of an XOR gate is 0 unless both inputs are 1. **(True/False)**
9. The NOR gate produces the opposite results of the XOR gate. **(True/False)**
10. A gate can be designed to accept more than two inputs. **(True/False)**
11. A transistor is made of semiconductor material. **(True/False)**
12. Inverting the output of an AND gate is equivalent to inverting the individual signals first, then passing them through an OR gate. **(True/False)**
13. The sum of two binary digits (ignoring the carry) is expressed by an AND gate. **(True/False)**
14. A full adder takes the carry-in value into account. **(True/False)**
15. A multiplexer adds all of the bits on its input lines to produce its output. **(True/False)**
16. Integrated circuits are classified by the number of gates contained in them. **(True/False)**
17. A CPU is an integrated circuit. **(True/False)**

## SECTION B

For Exercises 18 - 29, match the gate with the diagram or description of the operation.

- A. AND
- B. NAND
- C. XOR
- D. OR
- E. NOR
- F. NOT

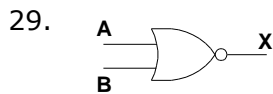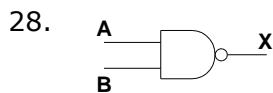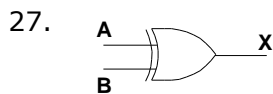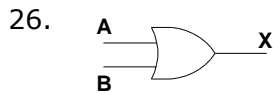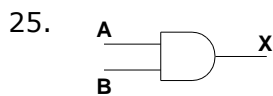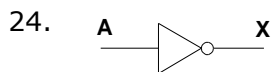
- 18. Inverts its input.
- 19. Produces a 1 only if all its inputs are 1 and a 0 otherwise.
- 20. Produces a 0 only if all its inputs are 0 and a 1 otherwise.
- 21. Produces a 0 only if its inputs are the same and a 1 otherwise.
- 22. Produces a 0 if all its inputs are all 1 and a 1 otherwise.
- 23. Produces a 1 if all its inputs are 0 and a 0 otherwise.



## SECTION C


**Exercises 30 - 47 are short answer or design questions.**

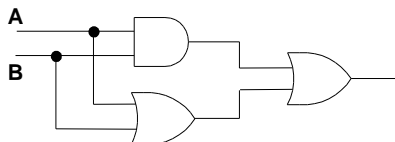30. Distinguish between a gate and a circuit.
31. What are the three notational methods for describing the behavior of gates and circuits?
32. Characterize the notations asked for in Exercise 31.
33. How many input signals can a gate receive and output signals can a gate produce?
34. Name six types of gates.
35. Compare and contrast the AND gate and the NOR gate.
36. Draw and label the symbol for a three input AND gate, then show its behavior with a truth table.
37. Draw and label the symbol for a three-input OR gate, then show its behavior with a truth table.
38. How can gates be combined into circuits?
39. What are the two general categories of circuits and how do they differ?
40. Draw a circuit diagram corresponding to the following Boolean expression:  
 $(A + B)(B + C)$
41. Draw a circuit diagram corresponding to the following Boolean expression:  
 $(AB + C)D$
42. Draw a circuit diagram corresponding to the following Boolean expression:  
 $A'B + (B+C)'$
43. Draw a circuit diagram corresponding to the following Boolean expression:  
 $(AB)' + (CD)'$
44. Show the behavior of the following circuit with a truth table:




A	B	AB	A+B	AB + (A+B)

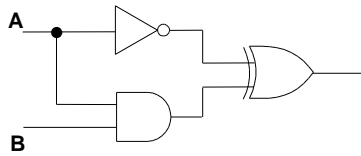45. Show the behavior of the following circuit with a truth table:




<b>A</b>	<b>B</b>	<b>A'</b>	<b>AB</b>	<b>A' <math>\oplus</math> (AB)</b>

46. Show the behavior of the following circuit with a truth table:

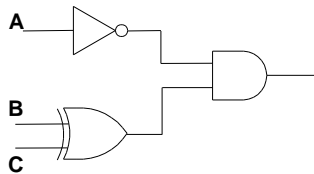[illegible]

47. Show the behavior of the following circuit with a truth table:

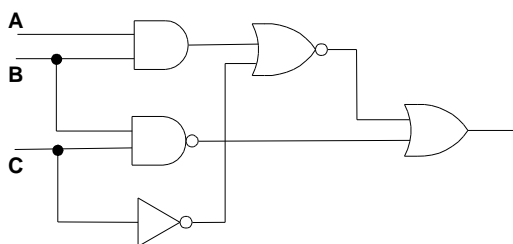[illegible]